

 


Lab 1 Report



Tuesday, February 15, 2022 2:56 PM

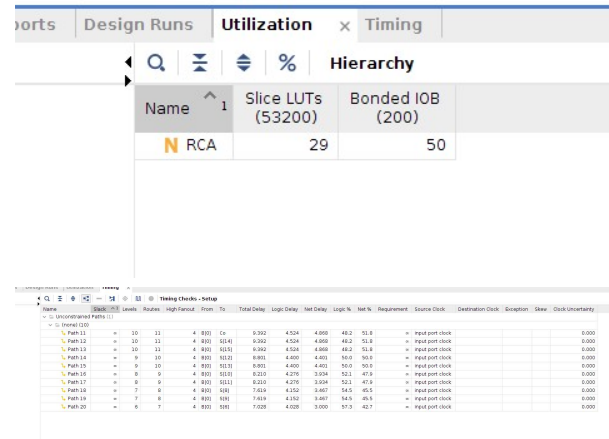

Add 2

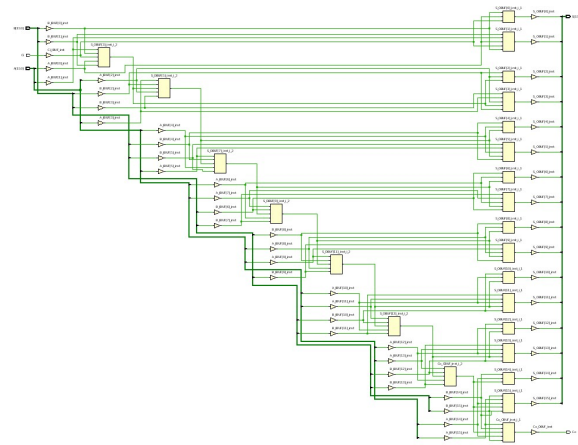

Add 4

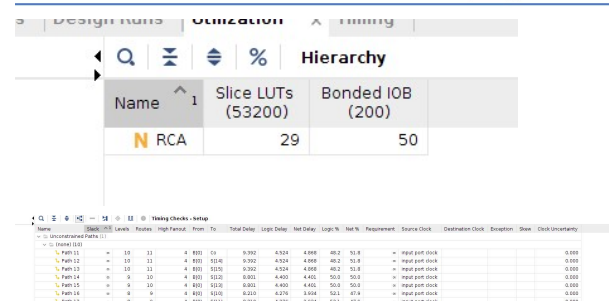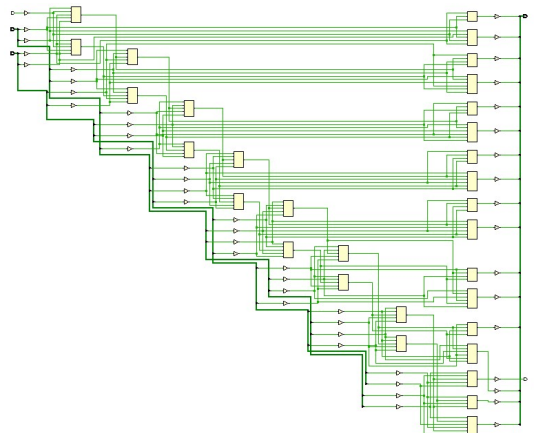

How does this data compare to the data found in Lab 1 (where we used 1 unit gate delay per logic gate and area of one gate for each gate)?

This compares to data find in Lab 1 because there is no relatable trend to the data that we found in the simulation to the synthesis

Is the data similar (similar trends)? Why or why not?

There is no real relatable trend to the data because the amount of bits added in the adder doesn't change so the number of lookup tables should remain the same. The number of lookup tables may have changed in our case because how it was implemented.

How could you make the design faster than what is reported?

You could make the design faster by decreasing the amount of bits added in the circuit thus making the circuit smaller. You could also make a dedicated 16 bit adder and have the propagation delay of 3 for only one gate needed but designing this would be a nightmare to do with our methods that we have.

How could you make it smaller?

designing this would be a nightmare to do with our methods that we have.

How could you make it smaller?

You could use the ripple carry adder and decrease the amount of adders needed to solve your problem

Given a specification for an N-bit Adder design (for example given a WPD), what would be your approach to meeting the required specifications, area or delay?

It would depend on what is the priority. If speed is the priority then I would use a higher adder circuit for a fast circuit. If I need to design something that doesn't take up a lot of space then I would design the ripple carry adder. Somewhere in the middle of that is a good way to start your design with small area but somewhat fast speed.

```
-- rca_w_fa.vhd
-- Ripple Carry Adder with full adder subcomponent

-----

library IEEE,WORK;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity FA is
    port( A,B,Ci: in std_logic;
          Co,S: out std_logic);
end;

architecture FA_BEHAV of FA is
begin
    Co <= (A and B) or (A and Ci) or (B and Ci)
    -- pragma synthesis_off
    after 2 ns
    -- pragma synthesis_on
    ;
    S <= (A xor B) xor Ci
    -- pragma synthesis_off
    after 2 ns
    -- pragma synthesis_on
    ;
end;

-----

library IEEE,WORK;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity RCA is
    generic(N:integer:=16); -- defaults to a 16 bit adder
    port( A,B: in std_logic_vector(N-1 downto 0);
          Ci: in std_logic;
          Co: out std_logic;
          S: out std_logic_vector(N-1 downto 0));
end;

architecture RCA_STRUCT of RCA is

    -- declarative area

    component FA
        port(A,B,Ci:in std_logic;Co,S:out std_logic);
    end component;

    signal C:std_logic_vector(N downto 0);

begin

    -- instantiation area

    C(0) <= Ci;


    GI: for I in 0 to N-1 generate
        GI:FA port map(A => A(I),B => B(I), Ci => C(I),Co => C(I+1),S => S(I));
    end generate;

    Co <= C(N);

end;
```

Name	Source	Level	Route	High Period	From	To	Total Delay	Logic Delay	Net Delay	Logic %	Net %	Requirement	Source Clock	Destination Clock	Exception	State	Clock Uncertainty
Unconstrained Paths (1)																	
Path 10		10	11	4	R01	C1	0.002	0.004	0.006	40.2	51.8	=	input port clock				0.000
Path 11		10	11	4	R01	D14	0.002	0.004	0.006	40.2	51.8	=	input port clock				0.000
Path 12		10	11	4	R01	D15	0.002	0.004	0.006	40.2	51.8	=	input port clock				0.000
Path 13		10	11	4	R01	D16	0.002	0.004	0.006	40.2	51.8	=	input port clock				0.000
Path 14		9	10	4	R01	D10	0.001	0.001	0.001	50.0	50.0	=	input port clock				0.000
Path 15		9	10	4	R01	D11	0.001	0.001	0.001	50.0	50.0	=	input port clock				0.000
Path 16		8	9	4	R01	D12	0.001	0.001	0.001	50.0	50.0	=	input port clock				0.000
Path 17		8	9	4	R01	D13	0.001	0.001	0.001	50.0	50.0	=	input port clock				0.000
Path 18		7	8	4	R01	D14	0.001	0.001	0.001	50.0	50.0	=	input port clock				0.000
Path 19		7	8	4	R01	D15	0.001	0.001	0.001	50.0	50.0	=	input port clock				0.000
Path 20		6	7	4	R01	D16	0.001	0.001	0.001	50.0	50.0	=	input port clock				0.000

Add 1

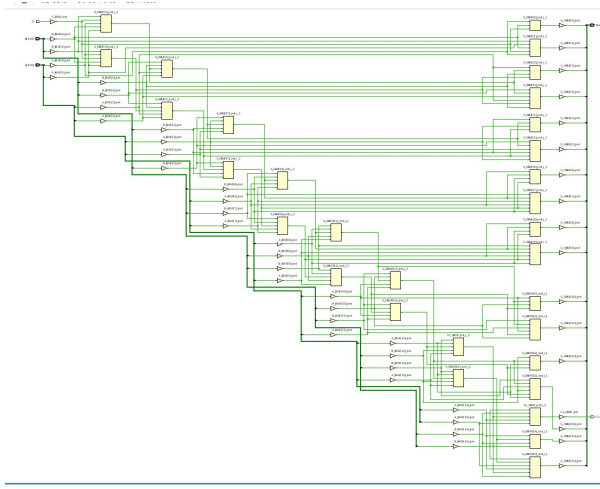

Name	1	Slice LUTs (53200)	Bonded IOB (200)
RCA		16	50

Name	Source	Level	Route	High Period	From	To	Total Delay	Logic Delay	Net Delay	Logic %	Net %	Requirement	Source Clock	Destination Clock	Exception	State	Clock Uncertainty
Unconstrained Paths (1)																	
Path 10		10	11	3	A00	C1	0.000	0.002	0.002	40.0	50.0	=	input port clock				0.000
Path 11		10	11	3	A00	D14	0.000	0.002	0.002	40.0	50.0	=	input port clock				0.000
Path 12		10	11	3	A00	D15	0.000	0.002	0.002	40.0	50.0	=	input port clock				0.000
Path 13		9	10	3	A00	D10	0.000	0.001	0.001	49.9	50.0	=	input port clock				0.000
Path 14		9	10	3	A00	D11	0.000	0.001	0.001	49.9	50.0	=	input port clock				0.000
Path 15		8	9	3	A00	D12	0.000	0.001	0.001	49.9	50.0	=	input port clock				0.000
Path 16		8	9	3	A00	D13	0.000	0.001	0.001	49.9	50.0	=	input port clock				0.000
Path 17		7	8	3	A00	D14	0.000	0.001	0.001	49.9	50.0	=	input port clock				0.000
Path 18		7	8	3	A00	D15	0.000	0.001	0.001	49.9	50.0	=	input port clock				0.000
Path 19		6	7	3	A00	D16	0.000	0.001	0.001	49.9	50.0	=	input port clock				0.000

```

-- rca_w_add2.vhd
-- ripple carry adder with 2-bit adder (ADD2) subcomponent
-- RCA generic integer N must be even (a multiple of 2)
-- what would be the limitation of N for RCA with ADD4 subcomponent

-----
-----
-----
library IEEE,WORK;
    use IEEE.STD_LOGIC_1164.ALL;
    use IEEE.STD_LOGIC_UNSIGNED.ALL;
-- ADD2 is a two-level logic (ignoring inverters) circuit that adds two, 2-bit numbers
-- you must design this block
entity ADD2 is
    port(
        A,B: in std_logic_vector(1 downto 0);
        Ci: in std_logic;
        Co: out std_logic;
        S: out std_logic_vector(1 downto 0));
end;

architecture ADD2_BEHAV of ADD2 is
begin
    Co <= (A(1) and B(1)) or (Ci and A(0) and B(1)) or (Ci and A(1) and A(0)) or (A(1) and A(0) and B(0)) or (Ci and A(1) and
B(0)) or (Ci and B(1) and B(0)) or (A(0) and B(1) and B(0))
    -- pragma synthesis_off
    after 2 ns
    -- pragma synthesis_on
    ;
    S(0) <= (not(Ci) and not(A(0)) and B(0)) or (not(Ci) and A(0) and not(B(0))) or (Ci and not(A(0)) and not(B(0))) or (Ci
and A(0) and B(0))
    -- pragma synthesis_off
    after 2 ns
    -- pragma synthesis_on
    ;
    S(1) <= (not(Ci) and not(A(1)) and not(A(0)) and B(1)) or (not(Ci) and not(A(1)) and B(1) and not(B(0))) or (not(A(1))
and not(A(0)) and B(1) and not(B(0))) or (not(Ci) and A(1) and not(A(0)) and not(B(1))) or (not(Ci) and A(1) and not(B(1))
and not(B(0))) or (A(1) and not(A(0)) and not(B(1)) and not(B(0))) or (not(A(1)) and A(0) and not(B(1)) and B(0)) or (Ci
and not(A(1)) and not(B(1)) and B(0)) or (Ci and not(A(1)) and A(0) and not(B(1))) or (A(1) and A(0) and B(1) and B(0)) or
(Ci and A(1) and B(1) and B(0)) or (Ci and A(1) and A(0) and B(1))
    -- pragma synthesis_off
    after 2 ns
    -- pragma synthesis_on
    ;
end;

-----
-----
-----
library IEEE,WORK;
    use IEEE.STD_LOGIC_1164.ALL;
    use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity RCA is
    generic(N:integer:=16);
    port(
        A,B: in std_logic_vector(N-1 downto 0);
        Ci: in std_logic;
        Co: out std_logic;
        S: out std_logic_vector(N-1 downto 0));
end;

architecture RCA_STRUCT of RCA is

    -- declarative area

    component ADD2
        port(A,B:in std_logic_vector(1 downto 0);Ci:in std_logic;Co:out std_logic;S:out std_logic_vector(1 downto 0));
    end component;

    signal C:std_logic_vector(N/2 downto 0);

begin

    -- it helps to draw this out and label the signal lines
    -- instantiation area

    C(0) <= Ci;

    GI: for I in 0 to N/2-1 generate
        GI:ADD2
            port map(A(1)>A(2*I+1),A(0)>A(2*I),B(1)>B(2*I+1),B(0)>B(2*I),Ci=>C(I),Co=>C(I+1),S(1)>S(2*I+1),S(0)>S(2*I));
    end generate;

    Co <= C(N/2);

end;

```

```

-- rca_w_add4.vhd
-- ripple carry adder with 2-bit adder (ADD4) subcomponent
-- RCA generic integer N must be even (a multiple of 4)
-- what would be the limitation of N for RCA with ADD4 subcomponent

-----
-----
-----
library IEEE,WORK;
    use IEEE.STD_LOGIC_1164.ALL;
    use IEEE.STD_LOGIC_UNSIGNED.ALL;
-- ADD2 is a two-level logic (ignoring inverters) circuit that adds two, 2-bit numbers
-- you must design this block
entity ADD4 is
    port(
        A,B: in std_logic_vector(3 downto 0);
        Ci: in std_logic;
        Co: out std_logic;
        S: out std_logic_vector(3 downto 0));
end;

architecture ADD4_BEHAV of ADD4 is
begin
    Co <= (A(3) and B(3)) or (A(3) and A(2) and B(2)) or (A(2) and B(3) and B(2)) or (A(3) and A(2) and A(1) and B(1))
or (A(2) and A(1) and B(3) and B(1)) or (A(3) and A(1) and B(2) and B(1)) or (A(1) and B(3) and B(2) and B(1)) or
(A(2) and A(1) and A(0) and B(3) and B(0)) or (A(3) and A(2) and A(1) and A(0) and B(0)) or (A(2) and A(1) and A(0)
and B(3) and Ci) or (A(3) and A(2) and A(1) and A(0) and Ci) or (A(3) and A(1) and A(0) and B(2) and B(0)) or (A(3)
and A(1) and A(0) and B(2) and Ci) or (A(3) and A(2) and A(0) and B(1) and B(0)) or (A(3) and A(2) and A(0) and B(1)
and Ci) or (A(3) and A(2) and A(1) and B(0) and Ci) or (A(2) and A(1) and B(3) and B(0) and Ci) or (A(3) and A(1) and
B(2) and B(0) and Ci) or (A(3) and A(2) and B(1) and B(0) and Ci) or (A(2) and A(0) and B(3) and B(1) and B(0)) or
(A(2) and A(0) and B(3) and B(1) and Ci) or (A(3) and A(0) and B(2) and B(1) and B(0)) or (A(3) and A(0) and B(2) and
B(1) and Ci) or (A(2) and B(3) and B(1) and B(0) and Ci) or (A(3) and B(2) and B(1) and B(0) and Ci) or (A(1) and
A(0) and B(3) and B(2) and B(0)) or (A(1) and A(0) and B(3) and B(2) and Ci) or (A(1) and B(3) and B(2) and B(0) and
Ci) or (A(0) and B(3) and B(2) and B(1) and B(0)) or (A(0) and B(3) and B(2) and B(1) and Ci) or (B(3) and B(2) and
B(1) and B(0) and Ci)
    -- pragma synthesis_off
    after 2 ns
    -- pragma synthesis_on
;
    S(0) <= (not(A(0)) and not(B(0)) and Ci) or (not(A(0)) and B(0) and not(Ci)) or (A(0) and not(B(0)) and not(Ci)) or
(A(0) and B(0) and Ci)
    -- pragma synthesis_off
    after 2 ns
    -- pragma synthesis_on
;
    S(1) <= (not(A(1)) and not(A(0)) and B(1) and not(B(0))) or (A(1) and not(A(0)) and not(B(1)) and not(B(0))) or
(not(A(1)) and not(A(0)) and B(1) and not(Ci)) or (A(1) and not(A(0)) and not(B(1)) and not(Ci)) or (not(A(1)) and
B(1) and not(B(0)) and not(Ci)) or (A(1) and not(B(1)) and not(B(0)) and not(Ci)) or (not(A(1)) and A(0) and
not(B(1)) and B(0)) or (not(A(1)) and A(0) and not(B(1)) and Ci) or (not(A(1)) and not(B(1)) and B(0) and Ci) or
(A(1) and A(0) and B(1) and B(0)) or (A(1) and A(0) and B(1) and Ci) or (A(1) and B(1) and B(0) and Ci)
    -- pragma synthesis_off
    after 2 ns
    -- pragma synthesis_on
;
    S(2) <= (not(A(2)) and not(A(1)) and B(2) and not(B(1))) or (A(2) and not(A(1)) and not(B(2)) and not(B(1))) or
(not(A(2)) and A(1) and not(B(2)) and B(1)) or (A(2) and A(1) and B(2) and B(1)) or (not(A(2)) and not(A(1)) and
not(A(0)) and B(2) and not(B(0))) or (A(2) and not(A(1)) and not(A(0)) and not(B(2)) and not(B(0))) or (not(A(2)) and
not(A(1)) and not(A(0)) and B(2) and not(Ci)) or (A(2) and not(A(1)) and not(A(0)) and not(B(2)) and not(Ci)) or
(not(A(2)) and not(A(1)) and B(2) and not(B(0)) and not(Ci)) or (A(2) and not(A(1)) and not(B(2)) and not(B(0)) and
not(Ci)) or (not(A(2)) and not(A(0)) and B(2) and not(B(1)) and not(B(0))) or (A(2) and not(A(0)) and not(B(2)) and
not(B(1)) and not(B(0)) and not(Ci)) or (not(A(2)) and not(A(0)) and B(2) and not(B(1)) and not(Ci)) or (A(2) and
not(B(2)) and not(B(1)) and not(Ci)) or (not(A(2)) and B(2) and not(B(1)) and not(B(0)) and not(Ci)) or (A(2) and
not(B(2)) and not(B(1)) and not(B(0)) and not(Ci)) or (not(A(2)) and A(1) and A(0) and not(B(2)) and B(0)) or
(not(A(2)) and A(1) and A(0) and not(B(2)) and Ci) or (not(A(2)) and A(1) and not(B(2)) and B(0) and Ci) or
(not(A(2)) and A(0) and not(B(2)) and B(1) and B(0)) or (not(A(2)) and A(0) and not(B(2)) and B(1) and Ci) or
(not(A(2)) and not(B(2)) and B(1) and B(0) and Ci) or (A(2) and A(1) and A(0) and B(2) and B(0)) or (A(2) and A(1)
and A(0) and B(2) and Ci) or (A(2) and A(1) and B(2) and B(0) and Ci) or (A(2) and A(0) and B(2) and B(1) and B(0))
or (A(2) and A(0) and B(2) and B(1) and Ci) or (A(2) and B(2) and B(1) and B(0) and Ci)
    -- pragma synthesis_off
    after 2 ns
    -- pragma synthesis_on
;
    S(3) <= (not(A(3)) and not(A(2)) and B(3) and not(B(2))) or (A(3) and not(A(2)) and not(B(3)) and not(B(2))) or
(not(A(3)) and A(2) and not(B(3)) and B(2)) or (A(3) and A(2) and B(3) and B(2)) or (not(A(3)) and not(A(2)) and
not(A(1)) and B(3) and not(B(1))) or (A(3) and not(A(2)) and not(A(1)) and not(B(3)) and not(B(1))) or (not(A(3)) and
not(A(1)) and B(3) and not(B(2)) and not(B(1))) or (A(3) and not(A(1)) and not(B(3)) and not(B(2)) and not(B(1))) or
(not(A(3)) and A(2) and A(1) and not(B(3)) and B(1)) or (A(3) and not(A(2)) and A(1) and not(B(3)) and B(1)) or (A(3)
and A(2) and A(1) and B(3) and B(1)) or (A(3) and A(1) and B(3) and B(2) and B(1)) or (not(A(3)) and not(A(2)) and
not(A(1)) and not(A(0)) and B(3) and not(B(0))) or (not(A(3)) and not(A(1)) and not(A(0)) and B(3) and not(B(2)) and
not(B(0))) or (A(3) and not(A(2)) and not(A(1)) and not(A(0)) and not(B(3)) and not(B(0))) or (A(3) and not(A(1)) and
not(A(0)) and not(B(3)) and not(B(0))) or (not(A(3)) and not(A(2)) and not(A(1)) and not(A(0)) and B(3) and
not(Ci)) or (not(A(3)) and not(A(1)) and not(A(0)) and B(3) and not(B(2)) and not(Ci)) or (A(3) and not(A(2)) and
not(A(1)) and not(A(0)) and not(Ci)) or (A(3) and not(A(1)) and not(A(0)) and not(B(3)) and not(B(0)) and not(B(2))
and not(Ci)) or (not(A(3)) and not(A(2)) and not(A(0)) and B(3) and not(B(1)) and not(B(0))) or (A(3) and not(A(2))
and not(A(0)) and not(B(3)) and not(B(1)) and not(B(0))) or (not(A(3)) and not(A(2)) and not(A(0)) and B(3) and
not(B(1)) and not(Ci)) or (A(3) and not(A(2)) and not(A(0)) and not(B(3)) and not(B(1)) and not(Ci)) or (not(A(3))
and not(A(2)) and not(A(1)) and B(3) and not(B(0)) and not(Ci)) or (A(3) and not(A(2)) and not(A(1)) and not(B(3))
and not(B(0)) and not(Ci)) or (not(A(3)) and not(A(1)) and B(3) and not(B(2)) and not(B(0)) and not(Ci)) or (A(3) and

```

```

not(A(1)) and not(B(3)) and not(B(2)) and not(B(0)) and not(Ci)) or (not(A(3)) and not(A(2)) and B(3) and not(B(1))
and not(B(0)) and not(Ci)) or (A(3) and not(A(2)) and not(B(3)) and not(B(1)) and not(B(0)) and not(Ci)) or
(not(A(3)) and not(A(0)) and B(3) and not(B(2)) and not(B(1)) and not(B(0))) or (A(3) and not(A(0)) and not(B(3)) and
not(B(2)) and not(B(1)) and not(B(0))) or (not(A(3)) and not(A(0)) and B(3) and not(B(2)) and not(B(1)) and not(Ci))
or (A(3) and not(A(0)) and not(B(3)) and not(B(2)) and not(B(1)) and not(Ci)) or (not(A(3)) and B(3) and not(B(2))
and not(B(1)) and not(B(0)) and not(Ci)) or (A(3) and not(B(3)) and not(B(2)) and not(B(1)) and not(B(0)) and
not(Ci)) or (not(A(3)) and A(1) and A(0) and not(B(3)) and B(2) and B(0)) or (not(A(3)) and A(2) and A(1) and A(0)
and not(B(3)) and B(0)) or (not(A(3)) and A(1) and A(0) and not(B(3)) and B(2) and Ci) or (not(A(3)) and A(2) and
A(1) and A(0) and not(B(3)) and Ci) or (not(A(3)) and A(2) and A(0) and not(B(3)) and B(1) and B(0)) or (not(A(3))
and A(2) and A(0) and not(B(3)) and B(1) and Ci) or (not(A(3)) and A(2) and A(1) and not(B(3)) and B(0) and Ci) or
(not(A(3)) and A(1) and not(B(3)) and B(2) and B(0) and Ci) or (not(A(3)) and A(2) and not(B(3)) and B(1) and B(0)
and Ci) or (not(A(3)) and A(0) and not(B(3)) and B(2) and B(1) and B(0)) or (not(A(3)) and A(0) and not(B(3)) and
B(2) and B(1) and Ci) or (not(A(3)) and not(B(3)) and B(2) and B(1) and B(0) and Ci) or (A(3) and A(1) and A(0) and
B(3) and B(2) and B(0)) or (A(3) and A(2) and A(1) and A(0) and B(3) and B(0)) or (A(3) and A(1) and A(0) and B(3)
and B(2) and Ci) or (A(3) and A(2) and A(1) and A(0) and B(3) and Ci) or (A(3) and A(2) and A(0) and B(3) and B(1)
and B(0)) or (A(3) and A(2) and A(0) and B(3) and B(1) and Ci) or (A(3) and A(2) and A(1) and B(3) and B(0) and Ci)
or (A(3) and A(1) and B(3) and B(2) and B(0) and Ci) or (A(3) and A(2) and B(3) and B(1) and B(0) and Ci) or (A(3)
and A(0) and B(3) and B(2) and B(1) and B(0)) or (A(3) and A(0) and B(3) and B(2) and B(1) and Ci) or (A(3) and B(3)
and B(2) and B(1) and B(0) and Ci)

```

```

-- pragma synthesis_off
after 2 ns
-- pragma synthesis_on

```

```

;

```

```

end;

```

```

-----
-----
-----

```

```

library IEEE,WORK;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity RCA is
generic(N:integer:=16);          -- defaults to a 16 bit adder
port(  A,B: in std_logic_vector(N-1 downto 0);
      Ci: in std_logic;
      Co: out std_logic;
      S: out std_logic_vector(N-1 downto 0));
end;

```

```

architecture RCA_STRUCT of RCA is

```

```

-- declarative area

```

```

component ADD4
port(A,B:in std_logic_vector(3 downto 0);Ci:in std_logic;Co:out std_logic;S:out std_logic_vector(3 downto 0));
end component;

```

```

signal C:std_logic_vector(N/4 downto 0);

```

```

begin

```

```

-- it helps to draw this out and label the signal lines
-- instantiation area

```

```

C(0) <= Ci;

```

```

GI: for I in 0 to N/4-1 generate

```

```

  GI:ADD4
  port map(
    A(0)=>A(4*I),
    A(1)=>A(4*I+1),
    A(2)=>A(4*I+2),
    A(3)=>A(4*I+3),
    B(0)=>B(4*I),
    B(1)=>B(4*I+1),
    B(2)=>B(4*I+2),
    B(3)=>B(4*I+3),
    Ci=>C(I),
    Co=>C(I+1),
    S(0)=>S(4*I),
    S(1)=>S(4*I+1),
    S(2)=>S(4*I+2),
    S(3)=>S(4*I+3));
end generate;

```

```

Co <= C(N/4);

```

```

end;

```

```

-- tb_RCA.vhd
-- this file can be used to simulate RCA adders.
-- instead of exhaustively simulating the adders,
-- this test bench picks random input vectors to test the adders
-- note limitations on N for the RCA subcomponents ...

```

```

library IEEE,STD,WORK;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
--use IEEE.STD_LOGIC_SIGNED.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.STD_LOGIC_TEXTIO.ALL;
use STD.TEXTIO.ALL;
use IEEE.MATH_REAL.ALL;

entity TB_RCA is
generic (
  N_ITS:integer:= 4000 ; -- number of random vectors for random TB
  N:integer:= 16 ; -- number of input bits for multiplier
  WPD:time:= 33 ns
);
end ;
-- the only change needed for each test bench is the wcpd above to account dor the different delays of the hardware design

architecture TB of TB_RCA is
file OUT_FILE: text
is out "sim_RCA.txt"; -- simulation output file
component RCA
generic(N:integer);
port(A,B: in std_logic_vector(N-1 downto 0);
  Ci: in std_logic;
  Co: out std_logic;
  S: out std_logic_vector(N-1 downto 0));
end component ;
signal A,B: std_logic_vector(N-1 downto 0);
signal S: std_logic_vector(N downto 0);
signal Ci: std_logic;
begin
  CUT:RCA -- Circuit Under Test
  generic map(N=>N)
  port map (A=>A,B=>B,Ci=>Ci,Co=>S(N),S=>S(N-1 downto 0));

  test_VECTOR : process
    variable I,Cin : integer;
    variable SEED_1,SEED_2,RN1,RN2 : integer := 0;
    variable R RAND : real;
  begin
    SEED_1 := 18; SEED_2 := 28; -- seeds for random number generator
    I := N_ITS-1; WH_LOOPPI : while I > -1 loop
      Cin := 0; WH_LOOPPC : while Cin < 2 loop -- 0 to 1
        -----
        UNIFORM(SEED_1,SEED_2,R RAND);
        RN1 := integer((2.0**31.0)**R RAND);
        RN1 := conv_integer(conv_std_logic_vector(RN1,N));
        UNIFORM(SEED_1,SEED_2,R RAND);
        RN2 := integer((2.0**31.0)**R RAND);
        RN2 := conv_integer(conv_std_logic_vector(RN2,N));
        A <= conv_std_logic_vector(RN1,N);
        B <= conv_std_logic_vector(RN2,N);
        if Cin = 1 then Ci <= '1'; else Ci <= '0'; end if;
        -----
        wait for WPD;
        Cin := Cin + 1;
      end loop WH_LOOPPC;
      I := I-1;
    end loop WH_LOOPPI;
    assert (false) report "sim done :)" severity FAILURE;
  end process;

  test_RCA : process
    variable OUTLINE : LINE;
    variable COMMA : string(1 to 3):= " , ";
    variable BLANK3 : string(1 to 3):= " ";
    variable BLANK1 : string(1 to 1):= " ";
    variable I,Cin : integer;
    variable S_INTEGER: integer;
  begin
    I := N_ITS-1; WH_LOOPPI : while I > -1 loop
      Cin := 0; WH_LOOPPC : while Cin < 2 loop -- 0 to 1
        wait for WPD;
        S_INTEGER := conv_integer(A) + conv_integer(B) + conv_integer(Ci);
        if conv_integer(S) /= S_INTEGER then
          WRITE(OUTLINE, A);
          WRITE(OUTLINE, '+');
          WRITE(OUTLINE, B);
          WRITE(OUTLINE, '=');
          WRITE(OUTLINE, S_INTEGER);
          WRITE(OUTLINE, '=');
          WRITE(OUTLINE, conv_std_logic_vector(S_INTEGER,N+1));
          WRITE(OUTLINE, BLANK3);
          WRITE(OUTLINE, '=');
          WRITE(OUTLINE, S);
          WRITE(OUTLINE, '=');
        end if;
      end loop WH_LOOPPC;
      I := I-1;
    end loop WH_LOOPPI;
  end process;
end architecture TB;

```

```
        WRITE(OUTLINE, conv_integer(S));
        WRITELINE(OUT_FILE, OUTLINE);
        assert (false) report "error :(" severity FAILURE;
    end if;
    Cin := Cin + 1;
end loop WH_LOOPC;
I := I-1;
end loop WH_LOOPI;
end process;

end ;

configuration CFG_TB of TB_RCA is
for TB
end for;
end ;
```